

ODEs: Applications of Separable Equations


Aamir Alaud Din, PhD

March 5, 2024

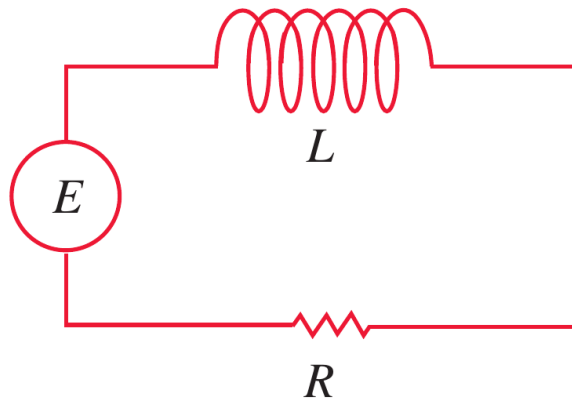Example-7 *LR-Series Circuit* (p-78, DGZ)

Kirchhoff's second law states that the sum of the voltage drop across the inductor ($L(di/dt)$) and the voltage drop across the resistor (iR) is the same as the impressed voltage ($E(t)$) on the circuit as shown in the figure below.

A 12-volt battery is connected to an *LR*-series circuit in which the inductance is 12 *henry* and the resistance is 10 *ohms*. Determine the current i if the initial current is zero.



Example-2 *LR-Series Circuit* (p-29, EK)

Kirchhoff's second law states that the sum of the voltage drop across the inductor ($L(di/dt)$) and the voltage drop across the resistor (iR) is the same as the impressed voltage ($E(t)$) on the circuit as shown in the figure below.

Model the RL-circuit in figure above and solve the resulting ODE for the current $i(t)$ A (amperes), where t is time. Assume that the circuit contains as an EMF $E(t)$ (electromotive force) a battery of $E = 48$ V (volts), which is constant, a resistor of $R = 11 \Omega$ (ohms), and an inductor of $L = 0.1$ H (henrys), and that the current is initially zero.

Example-3 *Hormone Level* (p-30, EK)

Assume that the level of a certain hormone in the blood of a patient varies with time. Suppose that the time rate of change is the difference between a sinusoidal input of a 24-hour period from the thyroid gland and a continuous removal rate proportional to the level present. Set up a model for the hormone level in the blood and find its general solution. Find the particular solution satisfying a suitable initial condition.

NOTE:

The students may be asked to solve a developed model with any method of instructor's choice.